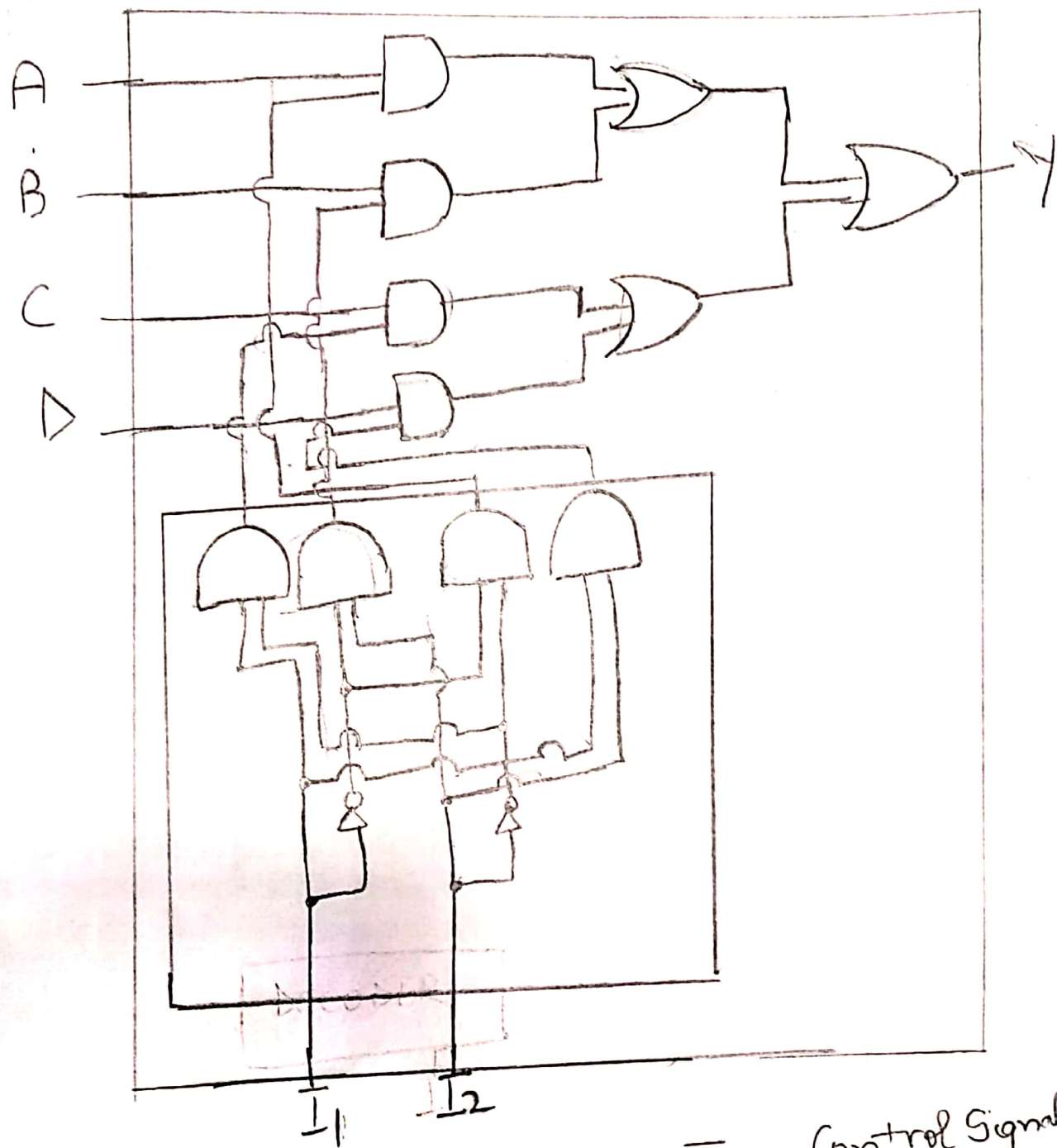


1.]



$\overline{I_1}$	$\overline{I_2}$	Y
0	0	A
0	1	B
1	0	C
1	1	D

$\overline{I_1}$ - Control Signal
 $\overline{I_2}$ - Control Signal

$$Y \Rightarrow ((\overline{I_1} \cdot \overline{I_2} \cdot A) + (\overline{I_1} \cdot I_2 \cdot B) + (I_1 \cdot \overline{I_2} \cdot C) + (I_1 \cdot I_2 \cdot D))$$


2.

x_2	x_1	x_0	f_1	f_2	f_3	f_4
0	0	0	0	0	1	0
0	0	1	0	1	1	0
0	1	0	0	1	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	1	0	0	1
1	1	0	1	0	0	1
1	1	1	0	1	0	1


Logic Equations:

$$\begin{aligned}
 f_1 &: \bar{x}_2 \cdot x_1 \cdot x_0 + x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0 \\
 f_2 &: \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + \bar{x}_2 \cdot x_1 \cdot \bar{x}_0 + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + x_2 \cdot x_1 \cdot x_0 \\
 f_3 &: \bar{x}_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + \bar{x}_2 \cdot x_1 \cdot \bar{x}_0 + \bar{x}_2 \cdot x_1 \cdot x_0 \\
 f_4 &: x_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0 + x_2 \cdot x_1 \cdot x_0
 \end{aligned}$$

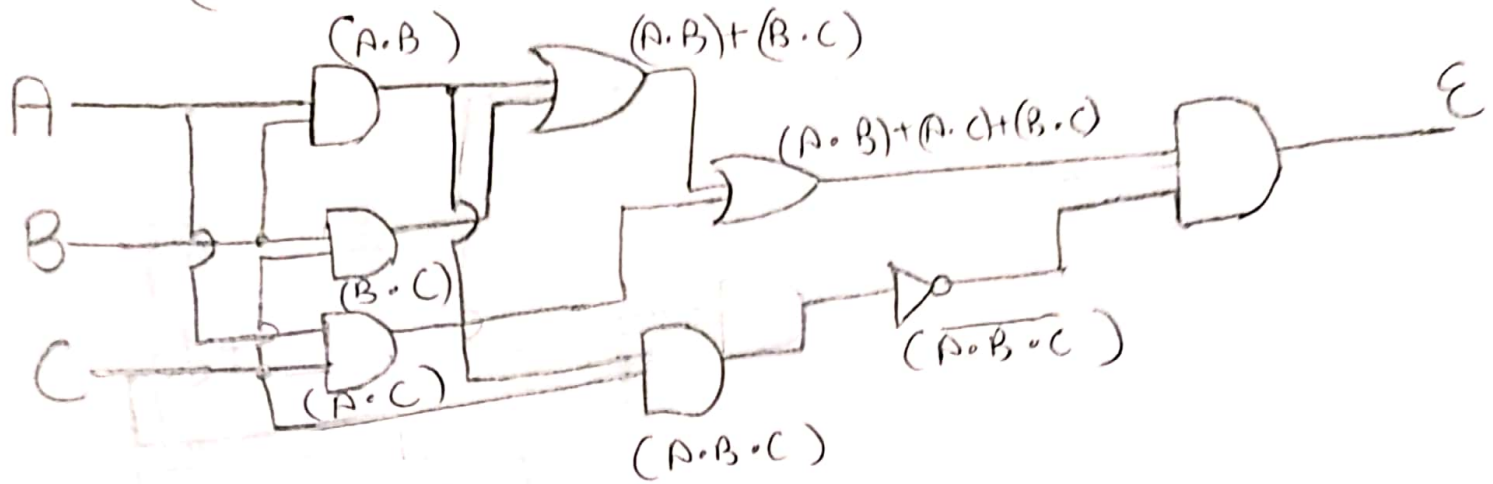3.] $E = ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A \cdot B \cdot C})$



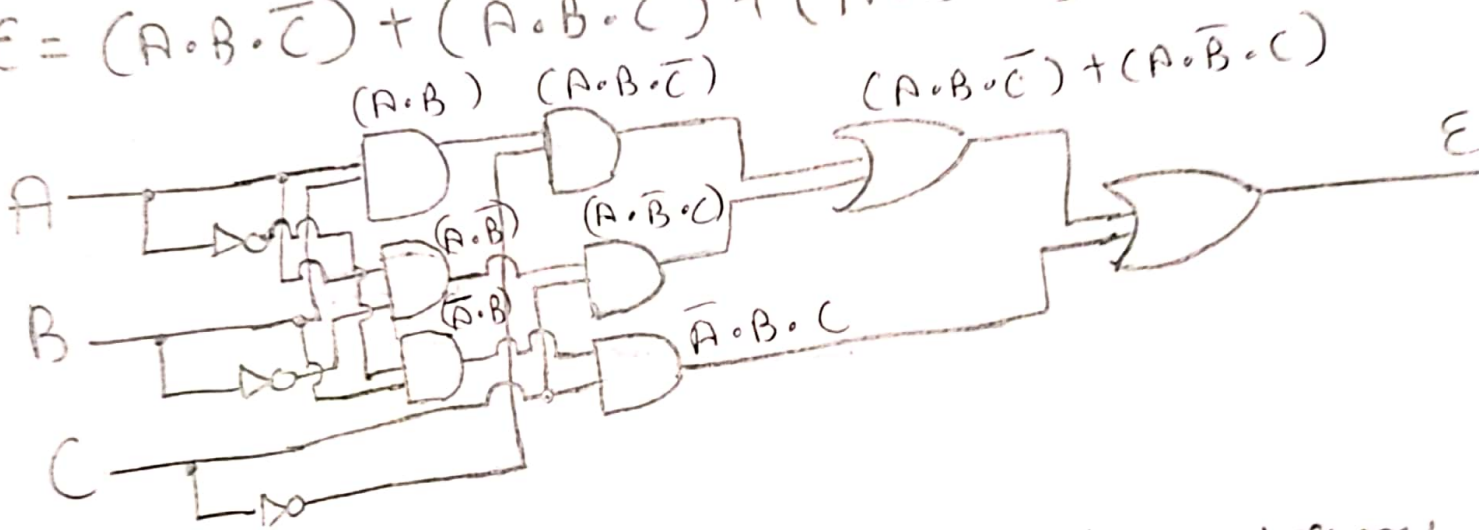$E = (A \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot C) + (\overline{A} \cdot B \cdot C)$



The first equation is more efficient in terms of the number of 2-input gates because it has a total of 7 gates whereas, equation two uses a total of 8 gates. Thus, less gates means low power usage, better performance and energy efficiency.

4.)

$$E = ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A \cdot B \cdot C})$$

$$\Rightarrow ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A} + \overline{B} + \overline{C}) \quad \left[\begin{array}{l} \text{De Morgan's law} \\ \overline{A \cdot B} = \overline{A} + \overline{B} \end{array} \right]$$

$$((A \cdot B) \cdot (\overline{A} + \overline{B} + \overline{C})) + ((A \cdot C) \cdot (\overline{A} + \overline{B} + \overline{C})) + ((B \cdot C) \cdot (\overline{A} + \overline{B} + \overline{C}))$$

$\textcircled{1}$ [Distributive law] $\textcircled{2}$ $\textcircled{3}$

$$\textcircled{1} \Rightarrow ((A \cdot B \cdot \overline{A}) + (A \cdot B \cdot \overline{B}) + (A \cdot B \cdot \overline{C})) \quad \left[\begin{array}{l} \text{Inverse law} \\ A \cdot \overline{A} = 0 \end{array} \right]$$

$$\textcircled{1} \Rightarrow (0 + 0 + (A \cdot B \cdot \overline{C}))$$

$$\textcircled{2} \Rightarrow ((A \cdot C \cdot \overline{A}) + (A \cdot C \cdot \overline{B}) + (A \cdot C \cdot \overline{C})) \quad \left[\begin{array}{l} \text{Inverse law} \\ A \cdot \overline{A} = 0 \end{array} \right]$$

$$\textcircled{2} \Rightarrow (0 + (A \cdot C \cdot \overline{B}) + 0)$$

$$\textcircled{3} \Rightarrow ((B \cdot C \cdot \overline{A}) + (B \cdot C \cdot \overline{B}) + (B \cdot C \cdot \overline{C})) \quad \left[\begin{array}{l} \text{Inverse law} \\ \overline{A} \cdot A = 0 \end{array} \right]$$

$$\textcircled{3} \Rightarrow ((B \cdot C \cdot \overline{A}) + 0 + 0)$$

\therefore , Putting $\textcircled{1}$, $\textcircled{2}$ & $\textcircled{3}$ back, we get

$$E = (A \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot C) + (\overline{A} \cdot B \cdot C) \quad \left[\begin{array}{l} \text{Commutative law} \\ A \cdot B = B \cdot A \end{array} \right]$$

Hence Proved

5.)

$$XOR = (A \cdot \bar{B}) + (\bar{A} \cdot B)$$

$$XOR = (A + B) \cdot (\overline{A \cdot B})$$

$$XOR = (A + B) \cdot (\overline{A \cdot B})$$

$$\Rightarrow (A + B) \cdot (\bar{A} + \bar{B})$$

[De Morgan's Law]
 $\overline{A \cdot B} = \bar{A} + \bar{B}$

$$\Rightarrow ((A \cdot \bar{A}) + (A \cdot \bar{B}) + (B \cdot \bar{A}) + (B \cdot \bar{B}))$$

$$\Rightarrow (0 + (A \cdot \bar{B}) + (\bar{A} \cdot B) + 0)$$

$$\Rightarrow (A \cdot \bar{B}) + (\bar{A} \cdot B)$$

[Inverse Law
 $A \cdot \bar{A} = 0$
Commutative Law
 $A \cdot B = B \cdot A$]


Hence Proved

6.)

A	B	C	XOR
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[XOR function
outputs 1 when
the true value
occurs in a
odd number]
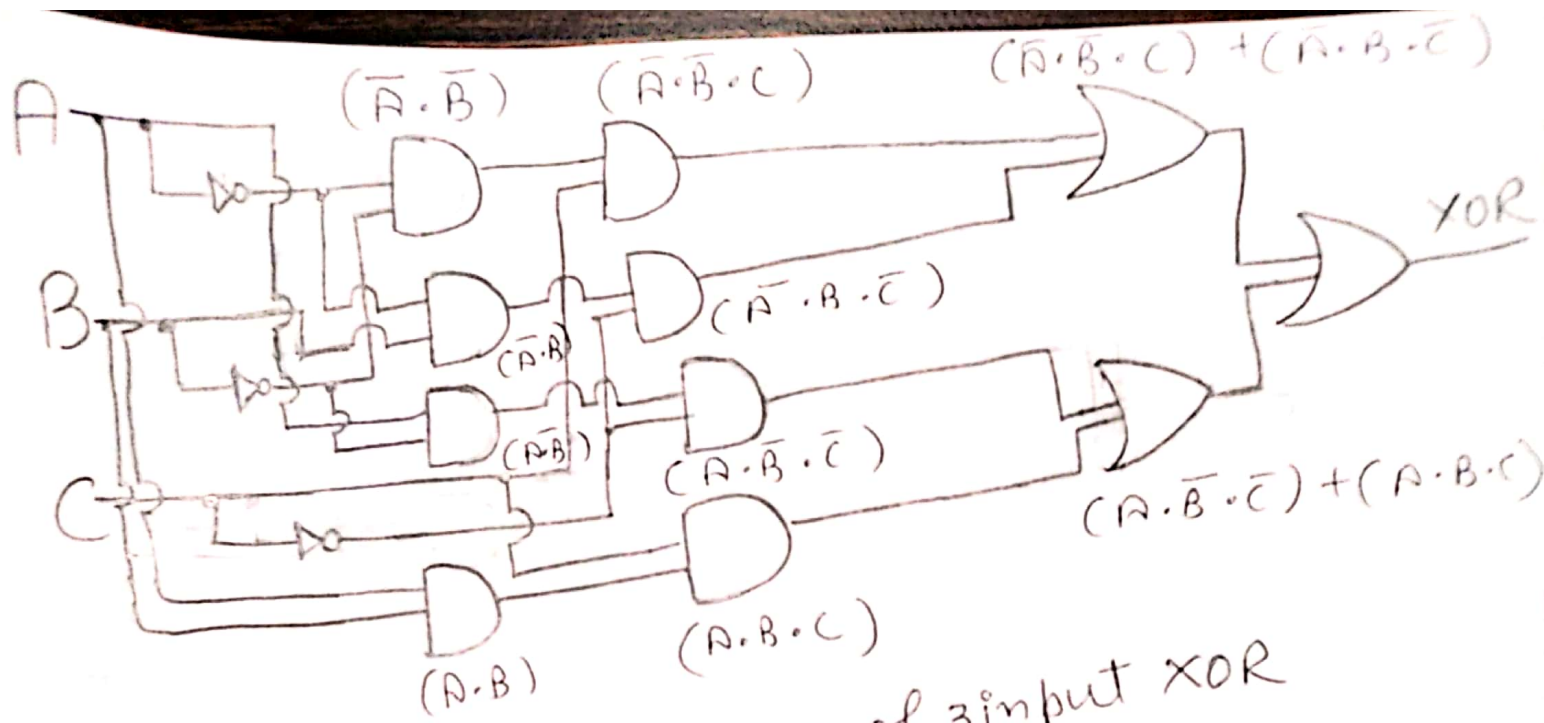
$$XOR = (\bar{A} \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B \cdot C)$$



Schematic Diagram of 3input XOR